



Lab 05 – Worksheet



Name: Mohib Ul Mehdi, Faaz Shahab, Basim Hussain

ID: fs09911,
mm09730,
mh09732

Section: T2

Task 1

Provide appropriately commented codes.

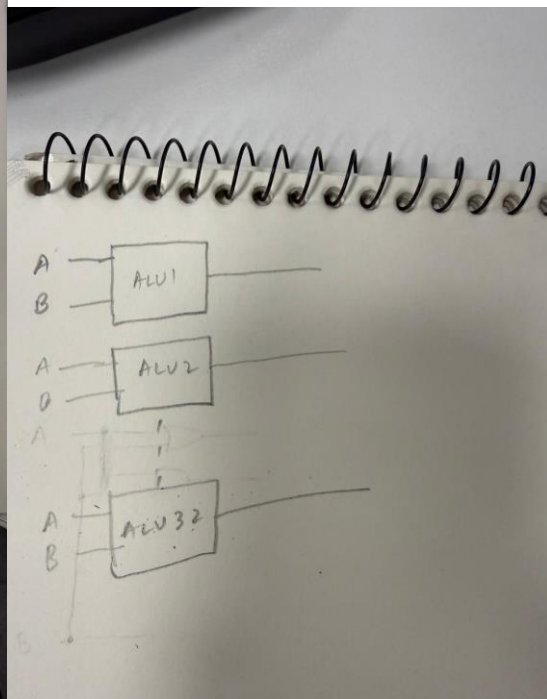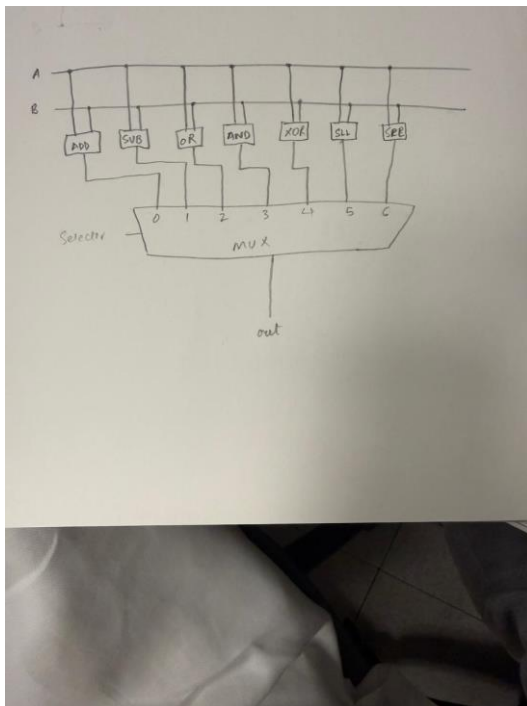



Task 2

Provide appropriately commented codes

ALU.v:

```
module ALU(input [31:0] A, input [31:0] B, input [3:0] ALUControl, output reg
[31:0] ALUResult, output Zero);
always @(*)
begin
    case(ALUControl)
        4'b0000: ALUResult = A + B;
        4'b0001: ALUResult = A - B;
        4'b0010: ALUResult = A & B;
        4'b0011: ALUResult = A | B;
        4'b0100: ALUResult = A ^ B;
        4'b0101: ALUResult = A << B[4:0];
        4'b0110: ALUResult = A >> B[4:0];
        default: ALUResult = 32'b0;
    endcase
end
assign Zero = (ALUResult == 0);
endmodule
```

ALU_tb.v:

```
module ALU_tb;

reg [31:0] A;
reg [31:0] B;
reg [3:0] ALUControl;
wire [31:0] ALUResult;
wire Zero;

ALU alusahab(A, B, ALUControl, ALUResult, Zero);

initial
begin
    // adding
    A = 10; B = 5; ALUControl = 4'b0000;
    #10;
    // subtracting
    A = 10; B = 5; ALUControl = 4'b0001;
    #10;
    // anding
    A = 10; B = 5; ALUControl = 4'b0010;
    #10;
    // oring
    A = 10; B = 5; ALUControl = 4'b0011;
    #10;
    // xoring
    A = 10; B = 5; ALUControl = 4'b0100;
```



```
#10;
// slling
A = 10; B = 2; ALUControl = 4'b0101;
#10;
// srling
A = 10; B = 2; ALUControl = 4'b0110;
#10;
end
endmodule
```

Add screenshot of your results



Comments

As we can see our A is 10 that is 1010 and B is 5 that is 0101 and then we perform all operations on it show in the waveform



Task 3


Provide appropriately commented codes

```
ALU.v:
module ALU(input [31:0] A, input [31:0] B, input [3:0] ALUControl, output reg
[31:0] ALUResult, output Zero);
always @(*)
begin
    case(ALUControl)
        4'b0000: ALUResult = A + B;
        4'b0001: ALUResult = A - B;
        4'b0010: ALUResult = A & B;
        4'b0011: ALUResult = A | B;
        4'b0100: ALUResult = A ^ B;
        4'b0101: ALUResult = A << B[4:0];
        4'b0110: ALUResult = A >> B[4:0];
        default: ALUResult = 32'b0;
    endcase
end
assign Zero = (ALUResult == 0);
endmodule
```




Add screenshots of your results

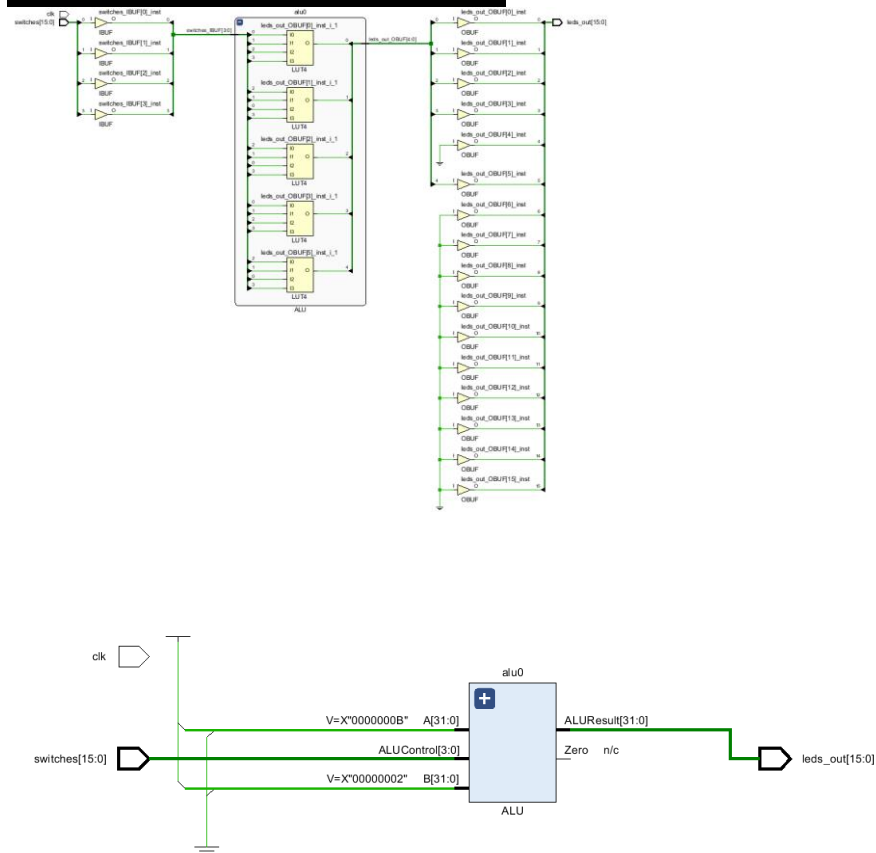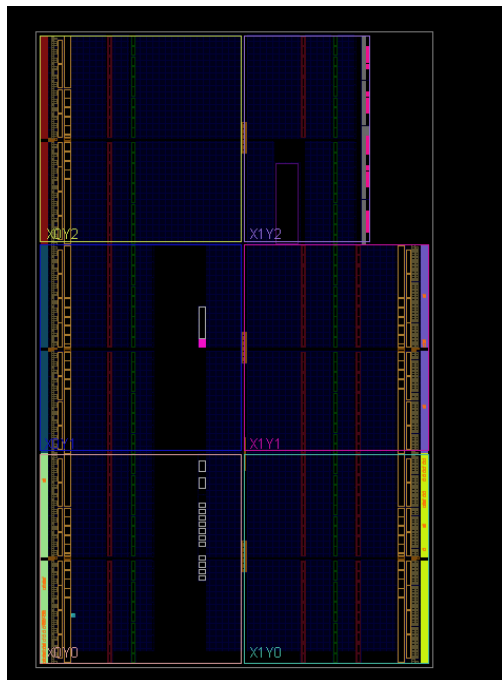

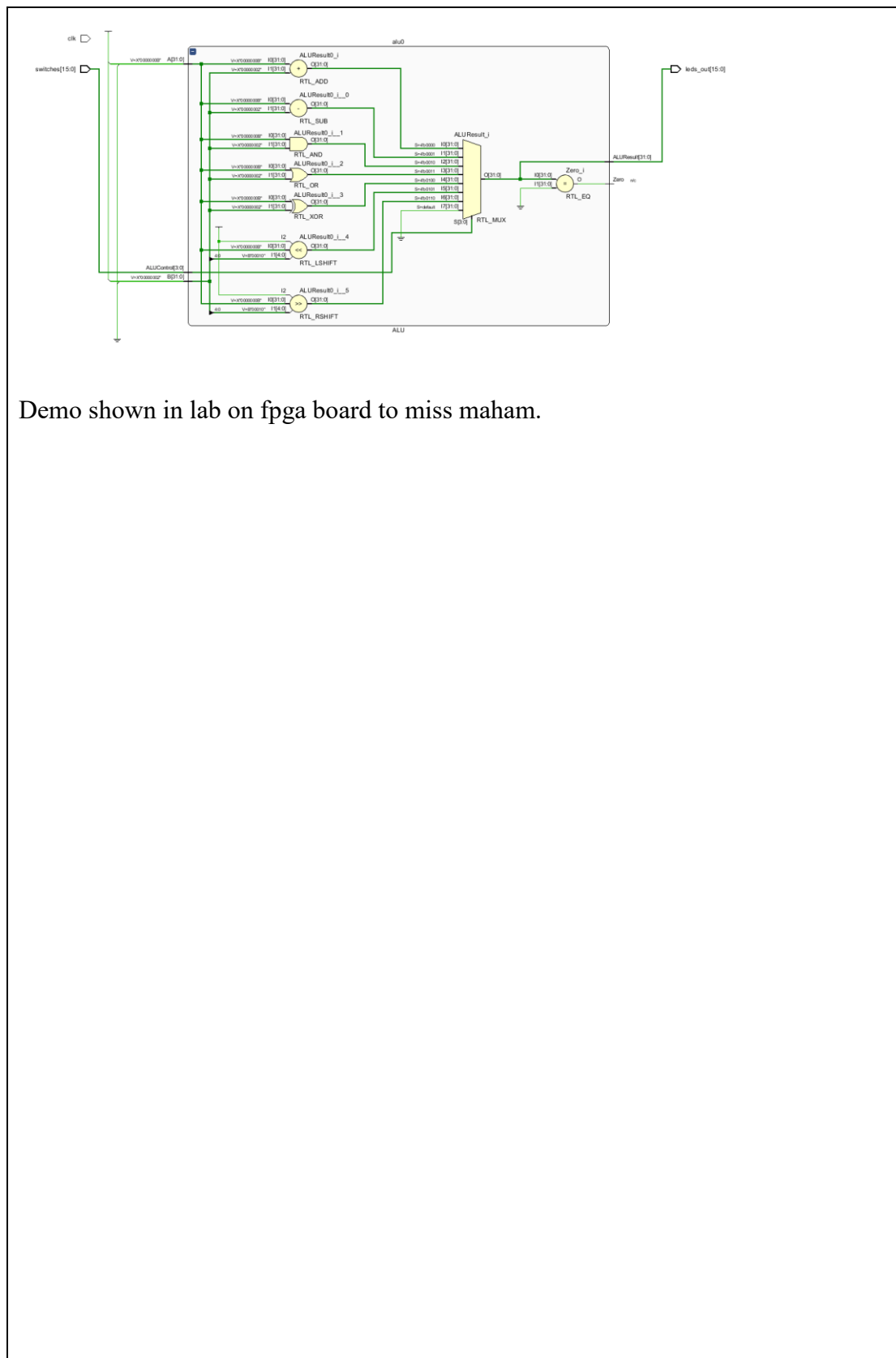

Demo shown in lab on fpga board to miss maham.